
CMPE 180-90

Lecture – FSM Factoring

(Ref: H&H Chapter 3, section 4)

Haluk Katircioglu
Computer Engineering Department
SJSU

Traffic Lights FSM Design

Design Components:

- T_A and T_B are sensors
- L_A and L_B are traffic lights
- Sensor indicates true if students are present and false if street is empty
- Each light receives digital inputs specifying whether it should be green, yellow or red.

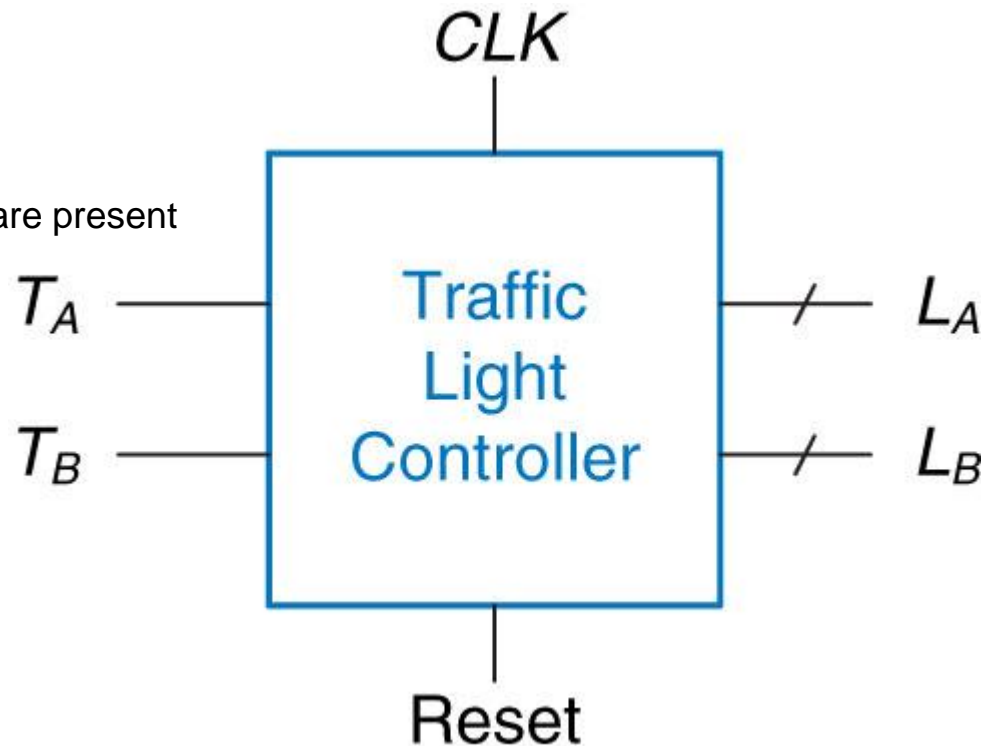


Figure 3.24 Black box view of finite state machine

Traffic Lights FSM Design

How it works:

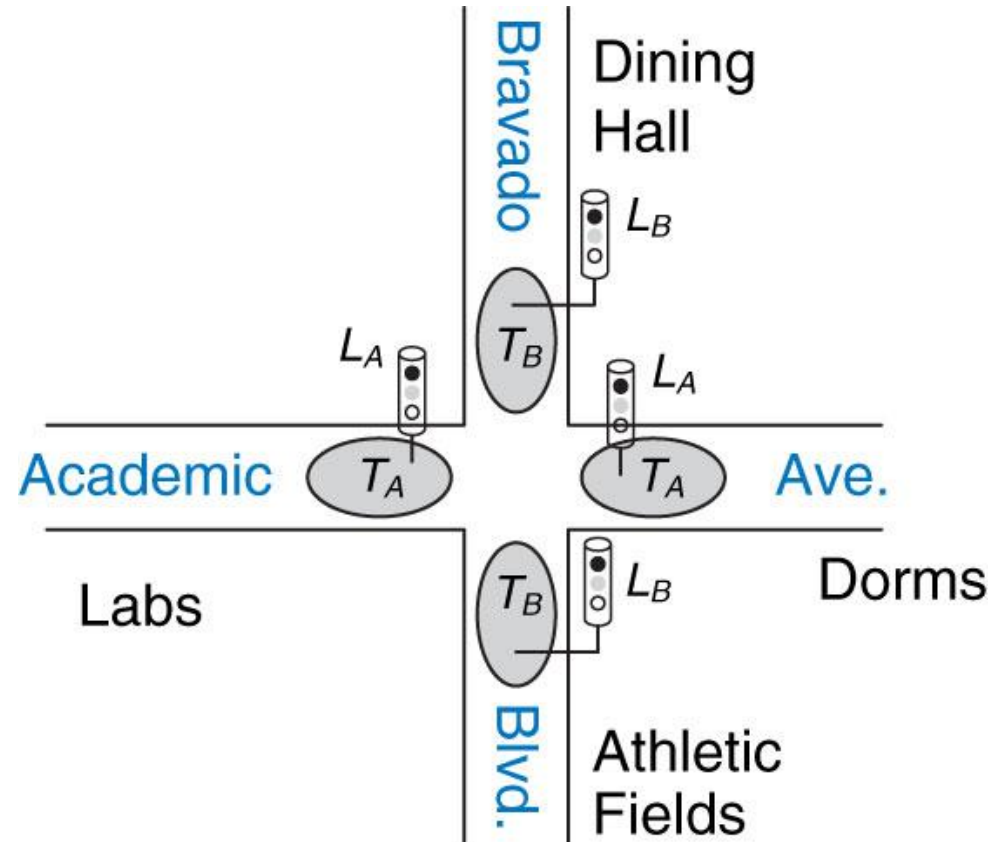


Figure 3.23 Campus map

Traffic Lights FSM Design

State Transition Diagram:

S0, S1, etc are states

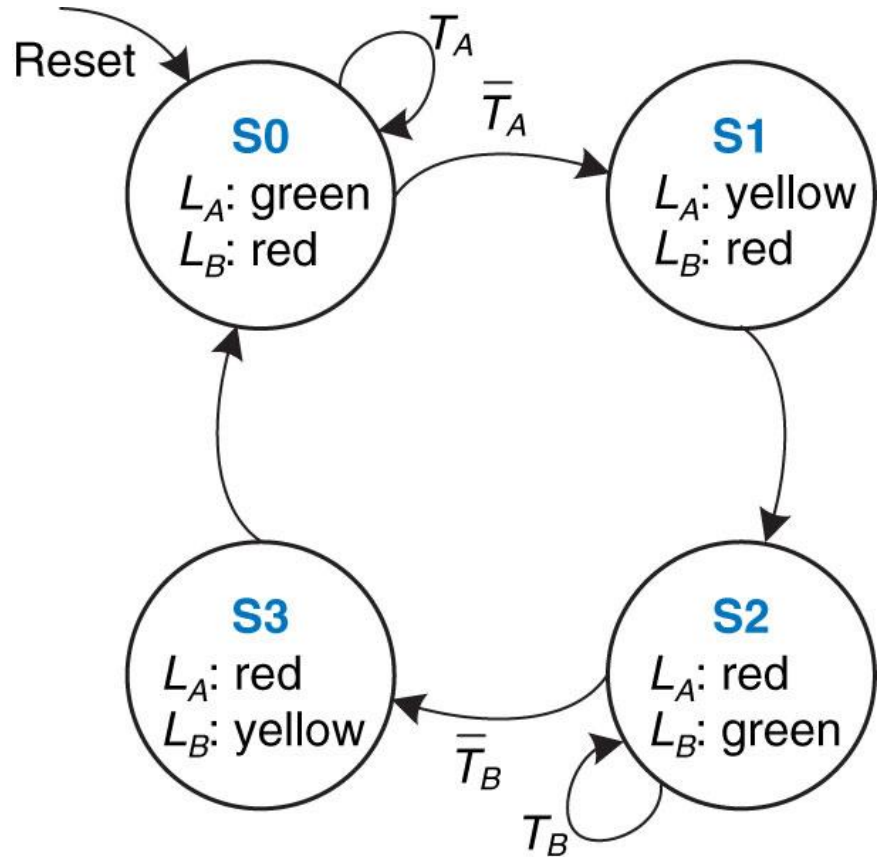
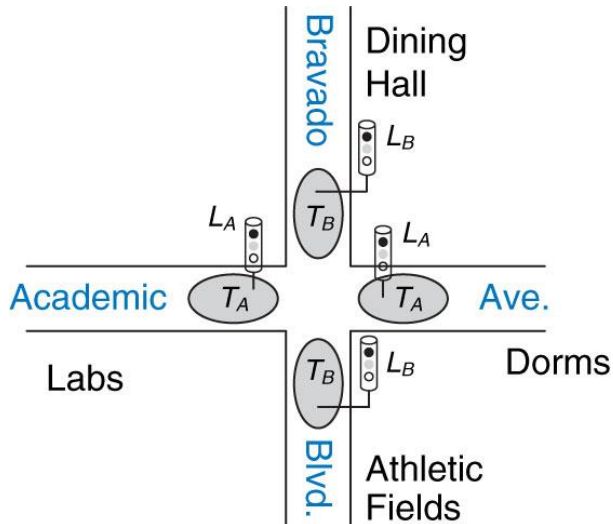


Figure 3.25 State transition diagram

Traffic Lights FSM Design

State Transition Table:

S_0, S_1, S_2, \dots are state bits

Current State	Inputs		Next State
S	T_A	T_B	S^+
S0	0	X	S1
S0	1	X	S0
S1	X	X	S2
S2	X	0	S3
S2	X	1	S2
S3	X	X	S0

Traffic Lights FSM Design


Current State		Inputs		Next State	
S_1	S_0	T_A	T_B	S^+_1	S^+_0
0	0	0	X	0	1
0	0	1	X	0	0
0	1	X	X	1	0
1	0	X	0	1	1
1	0	X	1	1	0
1	1	X	X	0	0

State	Encoding
S0	00
S1	01
S2	10
S3	11

FSM Encoded State Transition Table

Traffic Lights FSM Design

Lx1	Lx0	
0	0	GREEN
0	1	YELLOW
1	0	RED
1	1	don't care

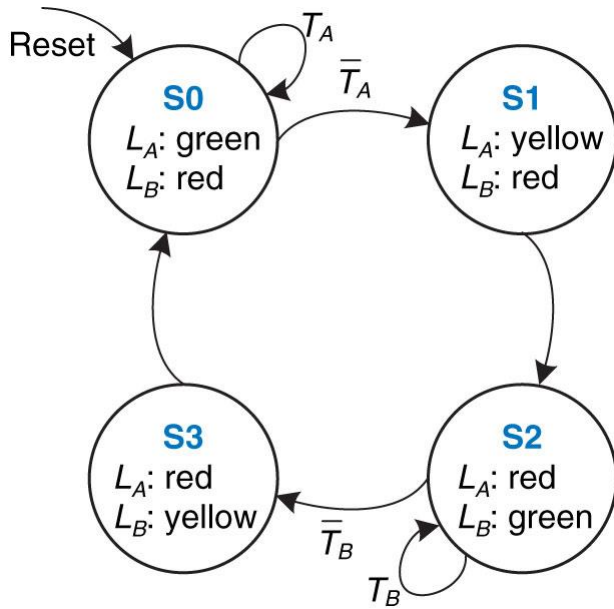

S ₁	S ₀	T _a	T _b	S ₁ ⁺	S ₀ ⁺	L _a 1	L _a 0	L _b 1	L _b 0
0	0	0	0	0	1	0	0	1	0
		0	1	0	1	0	0	1	0
		1	0	0	0	0	0	1	0
		1	1	0	0	0	0	1	0
0	1	0	0	1	0	0	1	1	0
		0	1	1	0	0	1	1	0
		1	0	1	0	0	1	1	0
		1	1	1	0	0	1	1	0
1	0	0	0	1	1	1	0	0	0
		0	1	1	0	1	0	0	0
		1	0	1	1	1	0	0	0
		1	1	1	0	1	0	0	0
1	1	0	0	0	0	1	0	0	1
		0	1	0	0	1	0	0	1
		1	0	0	0	1	0	0	1
		1	1	0	0	1	0	0	1

Traffic Lights FSM Design

$$D_1 = S_1 \oplus S_0$$


$$D_0 = \overline{S_1}\overline{S_0}\overline{T_A} + S_1\overline{S_0}\overline{T_B}$$

$$L_{A1} = S_1$$

$$L_{A0} = \overline{S_1}S_0$$

$$L_{B1} = \overline{S_1}$$

$$L_{B0} = S_1S_0$$

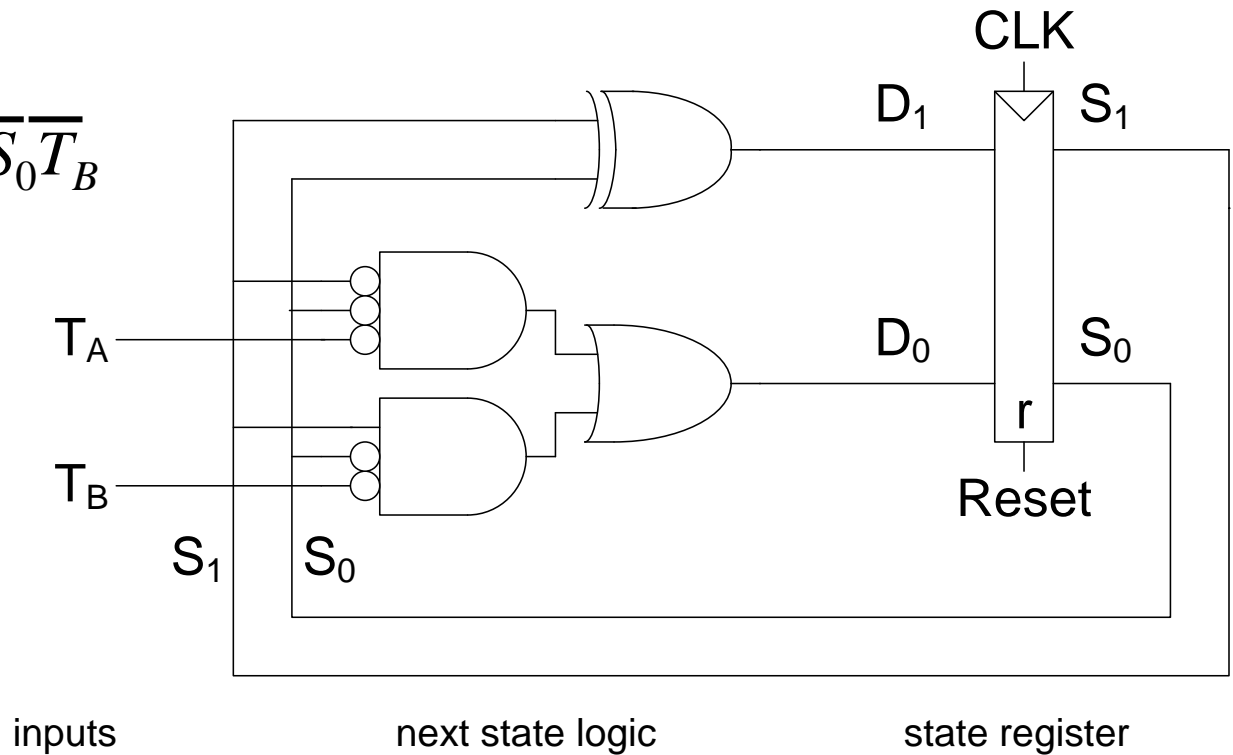


Traffic Lights FSM Design

$$L_{A1} = S_1$$

$$L_{A0} = \overline{S_1} S_0$$

$$L_{B1} = \overline{S_1}$$

$$L_{B0} = S_1 S_0$$

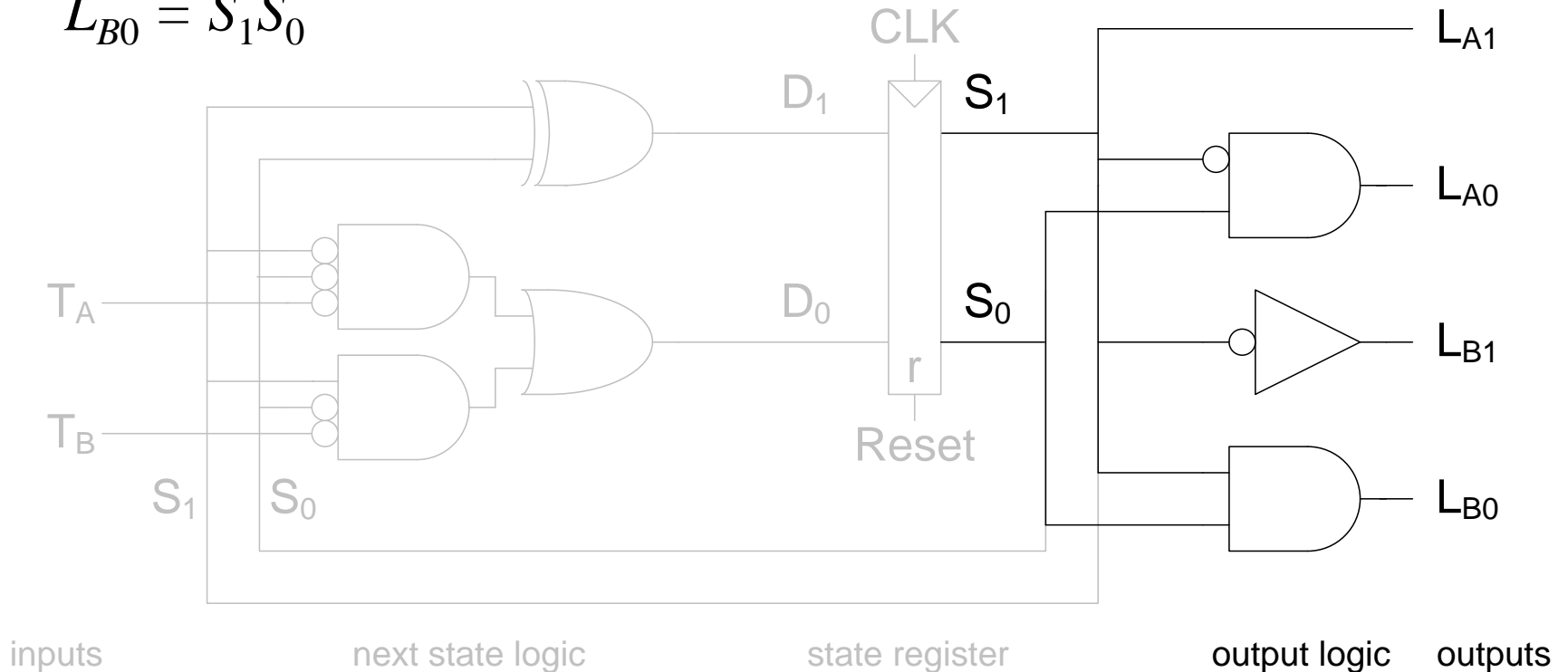

Factoring State Machines

Parade FSM


- Break complex FSMs into smaller interacting FSMs
- Example: Modify traffic light controller to have Parade Mode.
 - Two more inputs: P , R
 - When $P = 1$, enter Parade Mode & Bravado Blvd light stays green
 - When $R = 1$, leave Parade Mode

Parade FSM


Unfactored FSM




Factored FSM

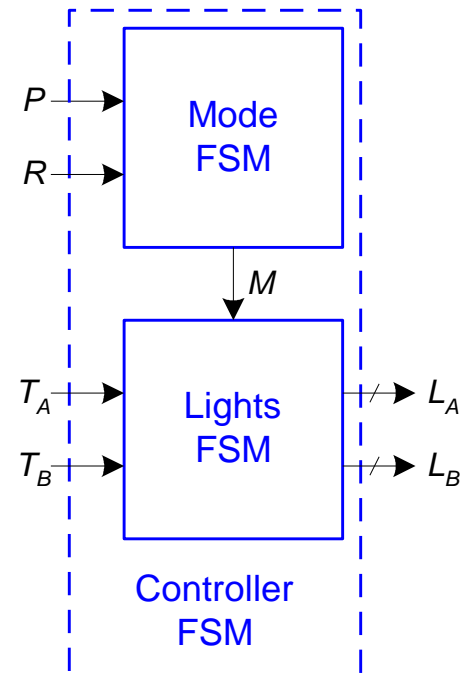


Unfactored FSM

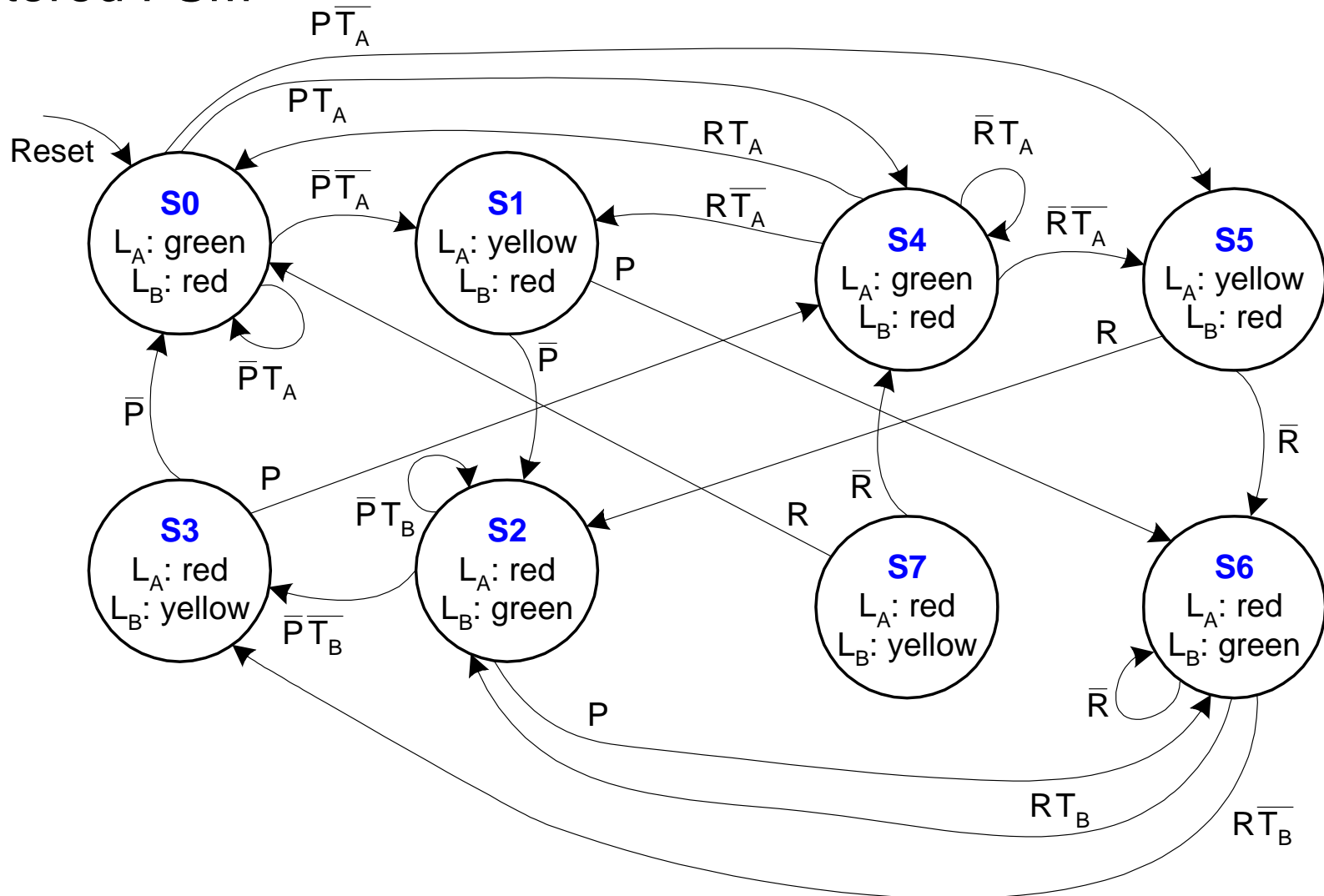

Factored FSM

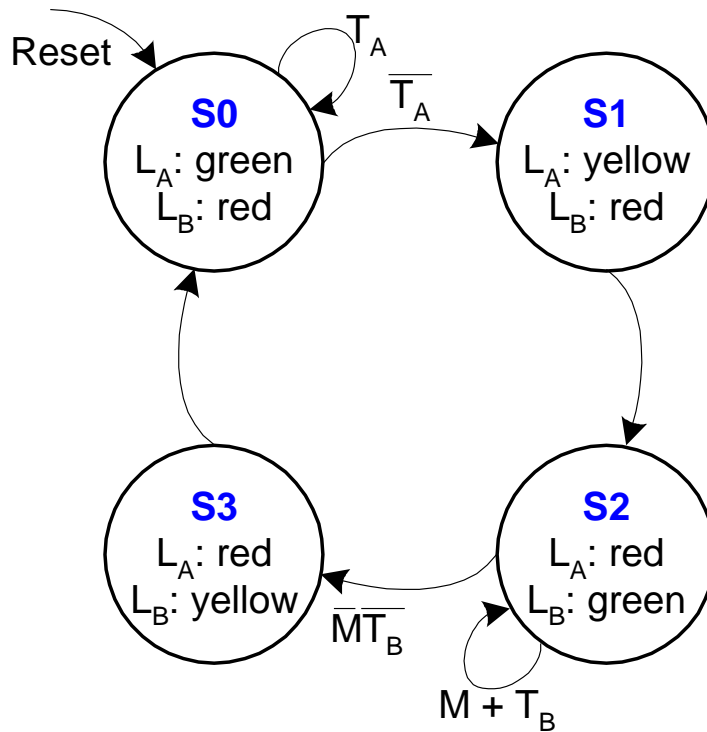

Lights FSM

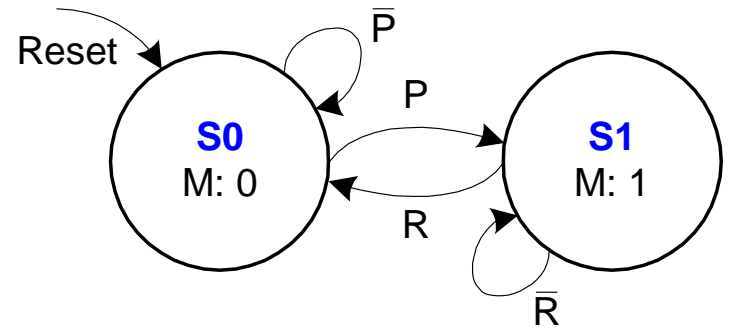

Mode FSM

Further improvements
in the design?